

**2.36** At an operating frequency of 300 MHz, it is desired to use a section of a lossless  $50\text{-}\Omega$  transmission line terminated in a short circuit to construct an equivalent load with reactance  $X = 40\text{ }\Omega$ . If the phase velocity of the line is  $0.75c$ , what is the shortest possible line length that would exhibit the desired reactance at its input? Verify your results using CD Module 2.5.

**Solution:**

$$\beta = \omega/u_p = \frac{(2\pi \text{ rad/cycle}) \times (300 \times 10^6 \text{ cycle/s})}{0.75 \times (3 \times 10^8 \text{ m/s})} = 8.38 \text{ rad/m}.$$

On a lossless short-circuited transmission line, the input impedance is always purely imaginary; i.e.,  $Z_{\text{in}}^{\text{sc}} = jX_{\text{in}}^{\text{sc}}$ . Solving Eq. (2.84) for the line length,

$$l = \frac{1}{\beta} \tan^{-1} \left( \frac{X_{\text{in}}^{\text{sc}}}{Z_0} \right) = \frac{1}{8.38 \text{ rad/m}} \tan^{-1} \left( \frac{40 \text{ }\Omega}{50 \text{ }\Omega} \right) = \frac{(0.675 + n\pi) \text{ rad}}{8.38 \text{ rad/m}},$$

for which the smallest positive solution is 8.05 cm (with  $n = 0$ ). Since  $u_p = 0.75c$ ,

$$\epsilon_{\text{eff}} = \left( \frac{c}{u_p} \right)^2 = 1.777.$$

From Module 2.5,  $Z(d) = j40\text{ }\Omega$  when

$$d = 0.107388\lambda.$$

But

$$\lambda = \frac{u_p}{f} = \frac{0.75 \times 3 \times 10^8}{3 \times 10^8} = 0.75 \text{ m}.$$

Hence,

$$d = 0.107388 \times 0.75 = 0.0805 \text{ m} = 8.05 \text{ cm}.$$

Options: Set Line and Load

$$d = 0$$

Page 1 of 1

frequency

(press Update to activate choice)

### Set Load

$$Z_0 = 50.0 \quad [\Omega]$$
$$\epsilon_r = 1.777777$$
$$l = 0.5 \text{ [ m ]}$$

Update

$$z_L = 0 + 0 [\Omega]$$

☒ Impedance    ☐ Admittance

Update