

2.32 A 6 m section of $150\ \Omega$ lossless line is driven by a source with

$$v_g(t) = 5 \cos(8\pi \times 10^7 t - 30^\circ) \quad (\text{V})$$

and $Z_g = 150\ \Omega$. If the line, which has a relative permittivity $\epsilon_r = 2.25$, is terminated in a load $Z_L = (150 - j50)\ \Omega$, determine:

- (a) λ on the line.
- (b) The reflection coefficient at the load.
- (c) The input impedance.
- (d) The input voltage \tilde{V}_i .
- (e) The time-domain input voltage $v_i(t)$.
- (f) Quantities in (a) to (d) using Modules 2.4 or 2.5.

Solution:

$$v_g(t) = 5 \cos(8\pi \times 10^7 t - 30^\circ) \text{ V},$$

$$\tilde{V}_g = 5e^{-j30^\circ} \text{ V}.$$

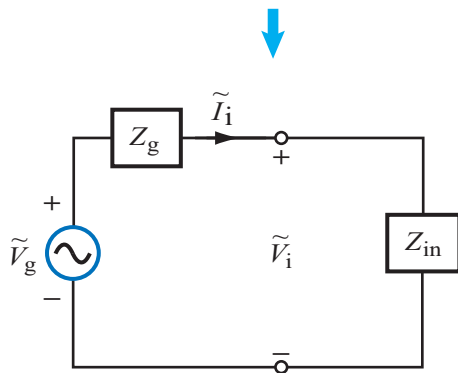
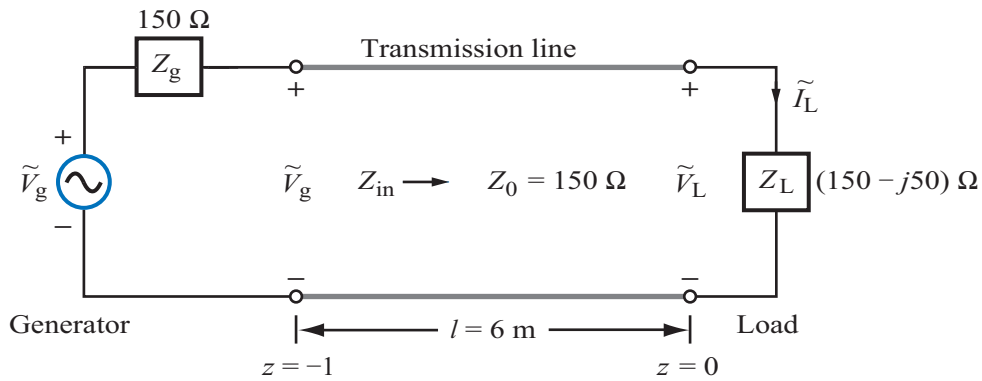


Figure P2.32 Circuit for Problem 2.32.

(a)

$$u_p = \frac{c}{\sqrt{\epsilon_r}} = \frac{3 \times 10^8}{\sqrt{2.25}} = 2 \times 10^8 \quad (\text{m/s}),$$

$$\lambda = \frac{u_p}{f} = \frac{2\pi u_p}{\omega} = \frac{2\pi \times 2 \times 10^8}{8\pi \times 10^7} = 5 \text{ m},$$

$$\beta = \frac{\omega}{u_p} = \frac{8\pi \times 10^7}{2 \times 10^8} = 0.4\pi \quad (\text{rad/m}),$$

$$\beta l = 0.4\pi \times 6 = 2.4\pi \quad (\text{rad}).$$

Since this exceeds 2π (rad), we can subtract 2π , which leaves a remainder $\beta l = 0.4\pi$ (rad).

(b) $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{150 - j50 - 150}{150 - j50 + 150} = \frac{-j50}{300 - j50} = 0.16e^{-j80.54^\circ}.$

(c)

$$Z_{\text{in}} = Z_0 \left[\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right]$$

$$= 150 \left[\frac{(150 - j50) + j150 \tan(0.4\pi)}{150 + j(150 - j50) \tan(0.4\pi)} \right] = (115.70 + j27.42) \Omega.$$

(d)

$$\tilde{V}_i = \frac{\tilde{V}_g Z_{\text{in}}}{Z_g + Z_{\text{in}}} = \frac{5e^{-j30^\circ} (115.7 + j27.42)}{150 + 115.7 + j27.42}$$

$$= 5e^{-j30^\circ} \left(\frac{115.7 + j27.42}{265.7 + j27.42} \right)$$

$$= 5e^{-j30^\circ} \times 0.44e^{j7.44^\circ} = 2.2e^{-j22.56^\circ} \quad (\text{V}).$$

(e)

$$v_i(t) = \Re[\tilde{V}_i e^{j\omega t}] = \Re[2.2e^{-j22.56^\circ} e^{j\omega t}] = 2.2 \cos(8\pi \times 10^7 t - 22.56^\circ) \text{ V}.$$

Module 2.4
Transmission Line Simulator
Options: Set Input / Output

d =
λ

$d = 1.2 \lambda = 6.0 \text{ m}$
 $Z_L = 150.0 - j 50.0 \ \Omega$

$Z_g = 150.0 + j 0.0 \ \Omega$
 $Z_0 = 150.0 + j 0.0 \ \Omega$
 $f = 40.0 \text{ MHz}$
 $\lambda = 5.0 \text{ m}$

$V_g = 4.33 - j 2.5 \text{ V}$
 $\epsilon_r = 2.25$

$d = 1.2 \lambda = 6.0 \text{ m}$
 $d = 0$

Set Line

Length units: ☐ [λ] ☒ [m]

Low Loss Approximation

Characteristic Impedance	$Z_0 =$	<input type="text" value="150"/>	Ω
Frequency	$f =$	<input type="text" value="4E7"/>	Hz
Relative Permittivity	$\epsilon_r =$	<input type="text" value="2.25"/>	
Line Length	$l =$	<input type="text" value="6"/>	[m]

$Z_L =$ + j Ω
☒ Impedance ☐ Admittance

Set Generator

 $V_g =$ + j V
 $Z_g =$ + j Ω

Output

Transmission Line Data 1

Cursor $d = 1.2 \lambda = 6.0 \text{ m}$

Impedance [Ω]	$Z(d) = 115.702409 + j 27.423507$ $= 118.907931 \angle 0.2327 \text{ rad}$
Admittance [S]	$Y(d) = 0.008183 - j 0.00194$ $= 0.00841 \angle -0.2327 \text{ rad}$
Reflection Coefficient	$\Gamma_d = -0.11718185 + j 0.11530585$ $= 0.16439899 \angle 2.364264 \text{ rad}$ $= 0.16439899 \angle 135.462322^\circ$
Voltage [V]	$V(d) = 2.055434 - j 0.853886$ $= 2.225742 \angle -0.3937 \text{ rad}$
Current [A]	$I(d) = 0.015164 - j 0.010974$ $= 0.018718 \angle -0.6265 \text{ rad}$
Power Flow [mW]	$P_{av} = 20.269378$

5 cos (-30)

5 sin(-30)