

**2.76** Repeat Problem 2.75 for the current  $I(z, t)$  on the line.

**Solution:**


$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = \frac{100 - 50}{100 + 50} = \frac{1}{3},$$


$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{25 - 50}{25 + 50} = \frac{-1}{3}.$$

From Eq. (2.149a),

$$I_1^+ = \frac{V_g}{R_g + Z_0} = \frac{60}{100 + 50} = 0.4 \text{ A}.$$

The bounce diagram is shown in Fig. P2.76(a) and  $I(t)$  in Fig. P2.76(b).

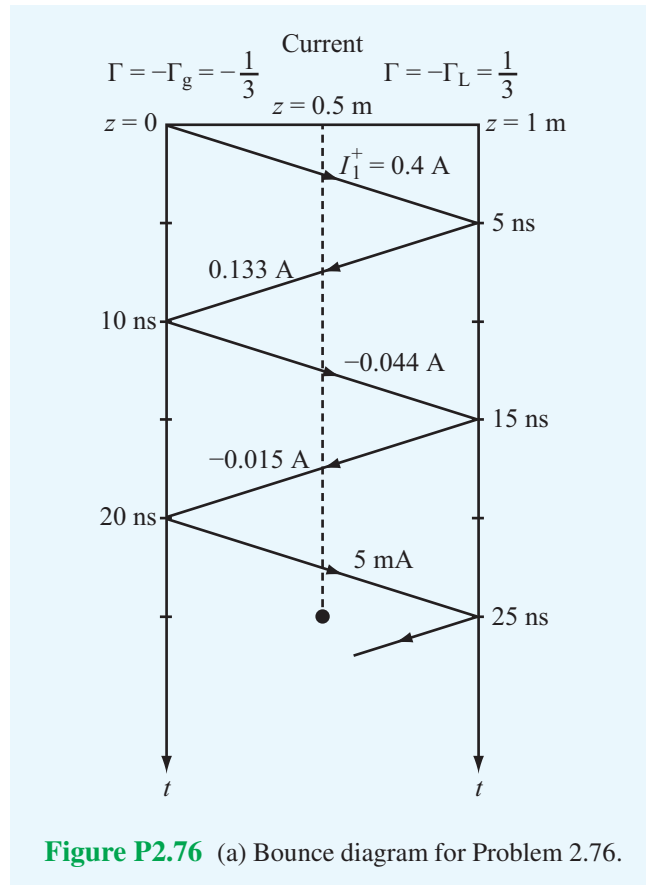

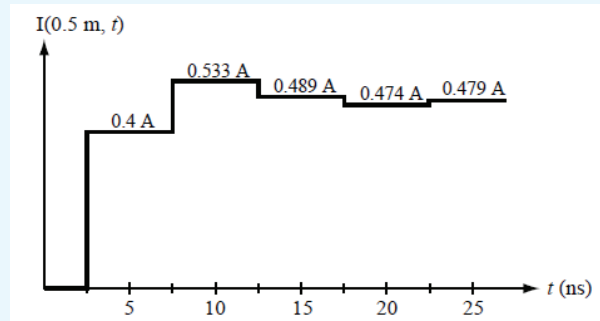

**Figure P2.76** (b) Time response of current.