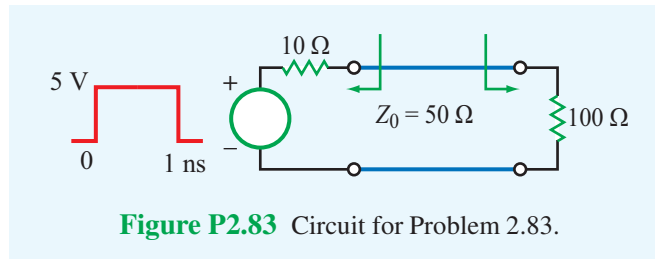


**2.83** The transmission-line circuit of **Fig. P2.83** is excited by a 1 ns long pulse that starts at  $t = 0$ . The line is 1 m long and the phase velocity of the line is  $2 \times 10^8$  m/s. Generate:

- (a) a plot of the voltage across the line at  $t = 6$  ns.
- (b) a plot of the voltage across the line at  $t = 12$  ns.
- (c) a plot of the voltage as a function of time at the sending end of the line.
- (d) a plot of the voltage as a function of time at the midpoint of the line.



**Solution:** The one-way propagation time is

$$T = \frac{l}{u_p} = \frac{1}{2 \times 10^8} = 5 \text{ ns.}$$

The voltage reflection coefficients at the generator and load ends of the line are

$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = \frac{10 - 50}{10 + 50} = -0.667,$$

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} = \frac{100 - 50}{100 + 50} = 0.33.$$

Also,

$$V_1^+ = \frac{V_{01} Z_0}{R_g + Z_0} = \frac{5 \times 50}{10 + 50} = 4.167 \text{ V.}$$