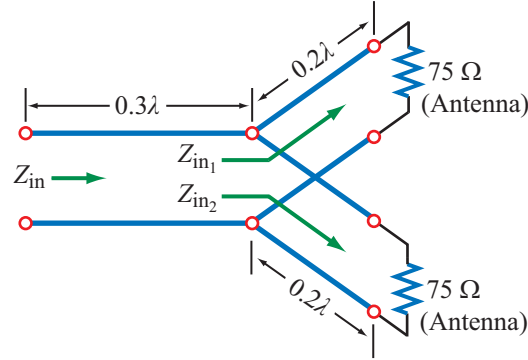


**Problem 2.33** Two half-wave dipole antennas, each with an impedance of  $75 \Omega$ , are connected in parallel through a pair of transmission lines, and the combination is connected to a feed transmission line, as shown in Fig. P2.33.



**Figure P2.33:** Circuit for Problem 2.33.

All lines are  $50 \Omega$  and lossless.

- Calculate  $Z_{in1}$ , the input impedance of the antenna-terminated line, at the parallel juncture.
- Combine  $Z_{in1}$  and  $Z_{in2}$  in parallel to obtain  $Z'_L$ , the effective load impedance of the feedline.
- Calculate  $Z_{in}$  of the feedline.

**Solution:**

(a)


$$Z_{in1} = Z_0 \left[ \frac{Z_{L1} + jZ_0 \tan \beta l_1}{Z_0 + jZ_{L1} \tan \beta l_1} \right]$$

$$= 50 \left\{ \frac{75 + j50 \tan[(2\pi/\lambda)(0.2\lambda)]}{50 + j75 \tan[(2\pi/\lambda)(0.2\lambda)]} \right\} = (35.20 - j8.62) \Omega.$$

(b)

$$Z'_L = \frac{Z_{in1} Z_{in2}}{Z_{in1} + Z_{in2}} = \frac{(35.20 - j8.62)^2}{2(35.20 - j8.62)} = (17.60 - j4.31) \Omega.$$

(c)

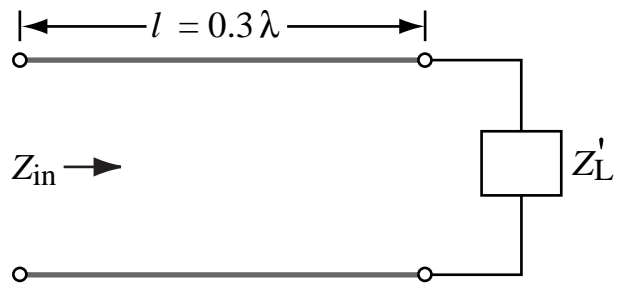

**Figure P2.33:** (b) Equivalent circuit.

$$Z_{\text{in}} = 50 \left\{ \frac{(17.60 - j4.31) + j50 \tan[(2\pi/\lambda)(0.3\lambda)]}{50 + j(17.60 - j4.31) \tan[(2\pi/\lambda)(0.3\lambda)]} \right\} = (107.57 - j56.7) \, \Omega.$$


---