

Problem 2.36 At an operating frequency of 300 MHz, it is desired to use a section of a lossless $50\text{-}\Omega$ transmission line terminated in a short circuit to construct an equivalent load with reactance $X = 40\text{ }\Omega$. If the phase velocity of the line is $0.75c$, what is the shortest possible line length that would exhibit the desired reactance at its input? Verify your results using CD Module 2.5.

Solution:

$$\beta = \omega/u_p = \frac{(2\pi \text{ rad/cycle}) \times (300 \times 10^6 \text{ cycle/s})}{0.75 \times (3 \times 10^8 \text{ m/s})} = 8.38 \text{ rad/m}.$$

On a lossless short-circuited transmission line, the input impedance is always purely imaginary; i.e., $Z_{\text{in}}^{\text{sc}} = jX_{\text{in}}^{\text{sc}}$. Solving Eq. (2.84) for the line length,

$$l = \frac{1}{\beta} \tan^{-1} \left(\frac{X_{\text{in}}^{\text{sc}}}{Z_0} \right) = \frac{1}{8.38 \text{ rad/m}} \tan^{-1} \left(\frac{40\text{ }\Omega}{50\text{ }\Omega} \right) = \frac{(0.675 + n\pi) \text{ rad}}{8.38 \text{ rad/m}},$$

for which the smallest positive solution is 8.05 cm (with $n = 0$). Since $u_p = 0.75c$,

$$\epsilon_{\text{eff}} = \left(\frac{c}{u_p} \right)^2 = 1.777.$$

From Module 2.5, $Z(d) = j40\text{ }\Omega$ when

$$d = 0.107388\lambda.$$

But

$$\lambda = \frac{u_p}{f} = \frac{0.75 \times 3 \times 10^8}{3 \times 10^8} = 0.75 \text{ m}.$$

Hence,

$$d = 0.107388 \times 0.75 = 0.0805 \text{ m} = 8.05 \text{ cm}.$$

Module 2.5 Wave and Input Impedance

Options: Set Line and Load

$Z =$ [Slider]

$d = 0.1073889 \lambda$

$Z_L = 0$ (Short Circuit)

$Z(d) = 0.0 + j 40.0 \Omega$

$Z_0 = 50.0 \Omega$

$\epsilon_r = 1.777777$

$d = 0.6666665 \lambda = 500.0 \text{ mm}$

$d = 0$

300.0 MHz [Slider] frequency

Choose length units: ☐ [λ] ☒ [m]
(press Update to activate choice)

Set Line

Characteristic Impedance $Z_0 =$ [50.0] [Ω]

Relative Permittivity $\epsilon_r =$ [1.777777]

Line Length $l =$ [0.5] [m]

Update

Set Load

$Z_L =$ [0] + [0] [Ω]

☒ Impedance ☐ Admittance

Update