

**Problem 2.40** A 100-MHz FM broadcast station uses a  $300\text{-}\Omega$  transmission line between the transmitter and a tower-mounted half-wave dipole antenna. The antenna impedance is  $73\text{ }\Omega$ . You are asked to design a quarter-wave transformer to match the antenna to the line.

- (a) Determine the electrical length and characteristic impedance of the quarter-wave section.
- (b) If the quarter-wave section is a two-wire line with  $D = 2.5\text{ cm}$ , and the wires are embedded in polystyrene with  $\epsilon_r = 2.6$ , determine the physical length of the quarter-wave section and the radius of the two wire conductors.

**Solution:**

(a) For a match condition, the input impedance of a load must match that of the transmission line attached to the generator. A line of electrical length  $\lambda/4$  can be used. From Eq. (2.97), the impedance of such a line should be

$$Z_0 = \sqrt{Z_{\text{in}} Z_L} = \sqrt{300 \times 73} = 148\text{ }\Omega.$$

(b)

$$\frac{\lambda}{4} = \frac{u_p}{4f} = \frac{c}{4\sqrt{\epsilon_r}f} = \frac{3 \times 10^8}{4\sqrt{2.6} \times 100 \times 10^6} = 0.465\text{ m},$$

and, from Table 2-2,

$$Z_0 = \frac{120}{\sqrt{\epsilon}} \ln \left[ \left( \frac{D}{d} \right) + \sqrt{\left( \frac{D}{d} \right)^2 - 1} \right] \text{ }\Omega.$$

Hence,

$$\ln \left[ \left( \frac{D}{d} \right) + \sqrt{\left( \frac{D}{d} \right)^2 - 1} \right] = \frac{148\sqrt{2.6}}{120} = 1.99,$$

which leads to

$$\left( \frac{D}{d} \right) + \sqrt{\left( \frac{D}{d} \right)^2 - 1} = 7.31,$$

and whose solution is  $D/d = 3.73$ . Hence,  $d = D/3.73 = 2.5\text{ cm}/3.73 = 0.67\text{ cm}$ .

---