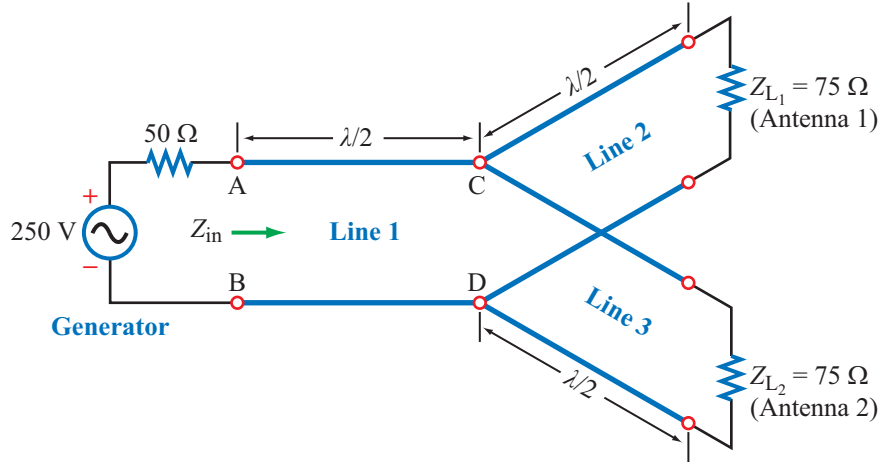


**Problem 2.43** If the two-antenna configuration shown in Fig. P2.43 is connected to a generator with  $\tilde{V}_g = 250$  V and  $Z_g = 50 \Omega$ , how much average power is delivered to each antenna?



**Figure P2.43:** Antenna configuration for Problem 2.43.

**Solution:** Since line 2 is  $\lambda/2$  in length, the input impedance is the same as  $Z_{L_1} = 75 \Omega$ . The same is true for line 3. At junction C–D, we now have two  $75\text{-}\Omega$  impedances in parallel, whose combination is  $75/2 = 37.5 \Omega$ . Line 1 is  $\lambda/2$  long. Hence at A–C, input impedance of line 1 is  $37.5 \Omega$ , and

$$\tilde{I}_i = \frac{\tilde{V}_g}{Z_g + Z_{in}} = \frac{250}{50 + 37.5} = 2.86 \text{ (A)},$$

$$P_{in} = \frac{1}{2} \Re[\tilde{I}_i \tilde{V}_i^*] = \frac{1}{2} \Re[\tilde{I}_i \tilde{I}_i^* Z_{in}^*] = \frac{(2.86)^2 \times 37.5}{2} = 153.37 \text{ (W)}.$$

This is divided equally between the two antennas. Hence, each antenna receives  $\frac{153.37}{2} = 76.68$  (W).