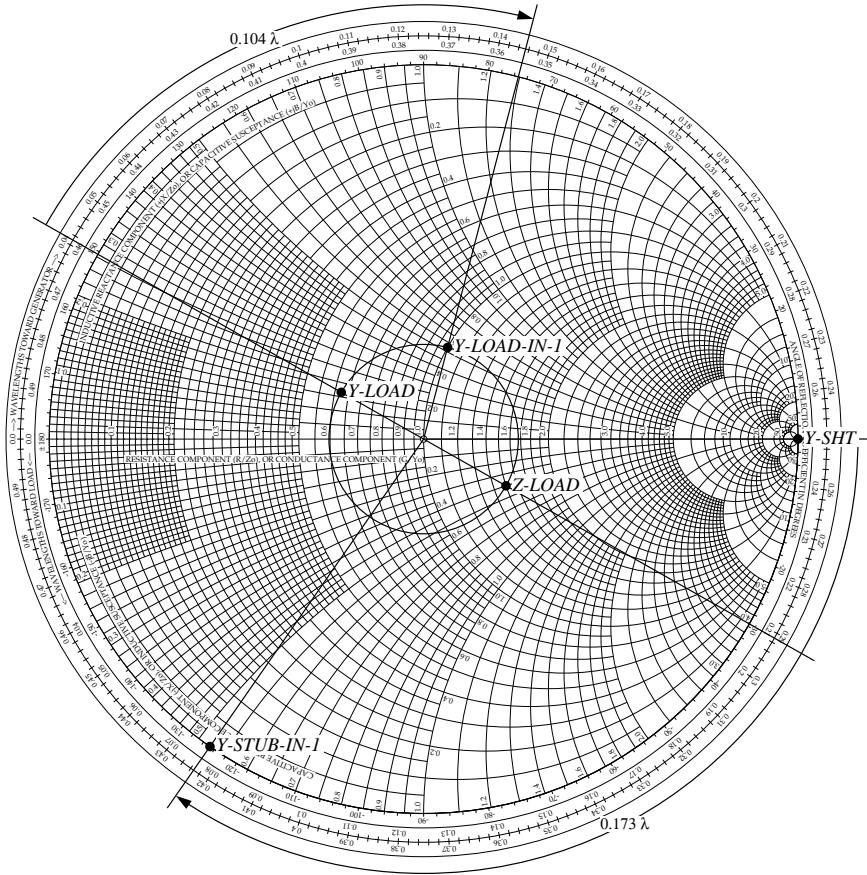


**Problem 2.68** A  $50\text{-}\Omega$  lossless line is to be matched to an antenna with  $Z_L = (75 - j20)\text{ }\Omega$  using a shorted stub. Use the Smith chart to determine the stub length and distance between the antenna and stub.




**Figure P2.68:** (a) First solution to Problem 2.68.

**Solution:** Refer to Fig. P2.68(a) and Fig. P2.68(b), which represent two different solutions.

$$z_L = \frac{Z_L}{Z_0} = \frac{(75 - j20)\text{ }\Omega}{50\text{ }\Omega} = 1.5 - j0.4$$

and is located at point *Z-LOAD* in both figures. Since it is advantageous to work in admittance coordinates,  $y_L$  is plotted as point *Y-LOAD* in both figures. *Y-LOAD* is at  $0.041\lambda$  on the WTG scale.

For the first solution in Fig. P2.68(a), point  $Y\text{-LOAD-IN-1}$  represents the point at which  $g = 1$  on the SWR circle of the load.  $Y\text{-LOAD-IN-1}$  is at  $0.145\lambda$  on the WTG scale, so the stub should be located at  $0.145\lambda - 0.041\lambda = 0.104\lambda$  from the load (or some multiple of a half wavelength further). At  $Y\text{-LOAD-IN-1}$ ,  $b = 0.52$ , so a stub with an input admittance of  $y_{\text{stub}} = 0 - j0.52$  is required. This point is  $Y\text{-STUB-IN-1}$  and is at  $0.423\lambda$  on the WTG scale. The short circuit admittance is denoted by point  $Y\text{-SHT}$ , located at  $0.250\lambda$ . Therefore, the short stub must be  $0.423\lambda - 0.250\lambda = 0.173\lambda$  long (or some multiple of a half wavelength longer).

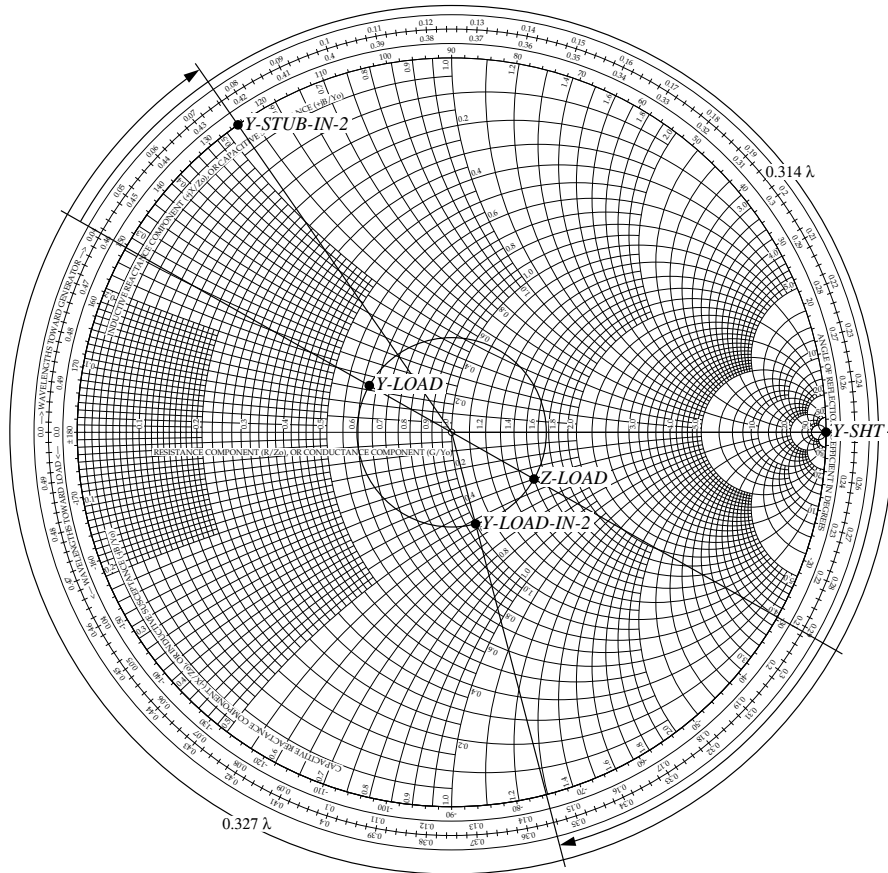

**Figure P2.68:** (b) Second solution to Problem 2.68.

For the second solution in Fig. P2.68(b), point  $Y\text{-LOAD-IN-2}$  represents the point at which  $g = 1$  on the SWR circle of the load.  $Y\text{-LOAD-IN-2}$  is at  $0.355\lambda$  on the WTG scale, so the stub should be located at  $0.355\lambda - 0.041\lambda = 0.314\lambda$  from the

load (or some multiple of a half wavelength further). At *Y-LOAD-IN-2*,  $b = -0.52$ , so a stub with an input admittance of  $y_{\text{stub}} = 0 + j0.52$  is required. This point is *Y-STUB-IN-2* and is at  $0.077\lambda$  on the WTG scale. The short circuit admittance is denoted by point *Y-SHT*, located at  $0.250\lambda$ . Therefore, the short stub must be  $0.077\lambda - 0.250\lambda + 0.500\lambda = 0.327\lambda$  long (or some multiple of a half wavelength longer).

---