
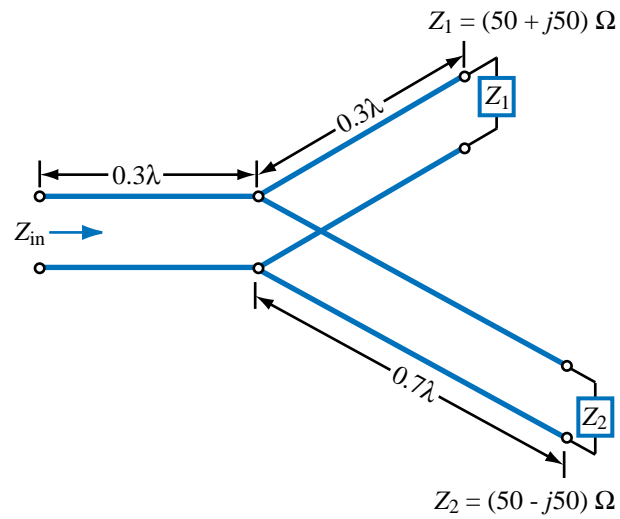


**Problem 2.72** Determine  $Z_{\text{in}}$  of the feed line shown in Fig. P2.72. All lines are lossless with  $Z_0 = 50 \, \Omega$ .

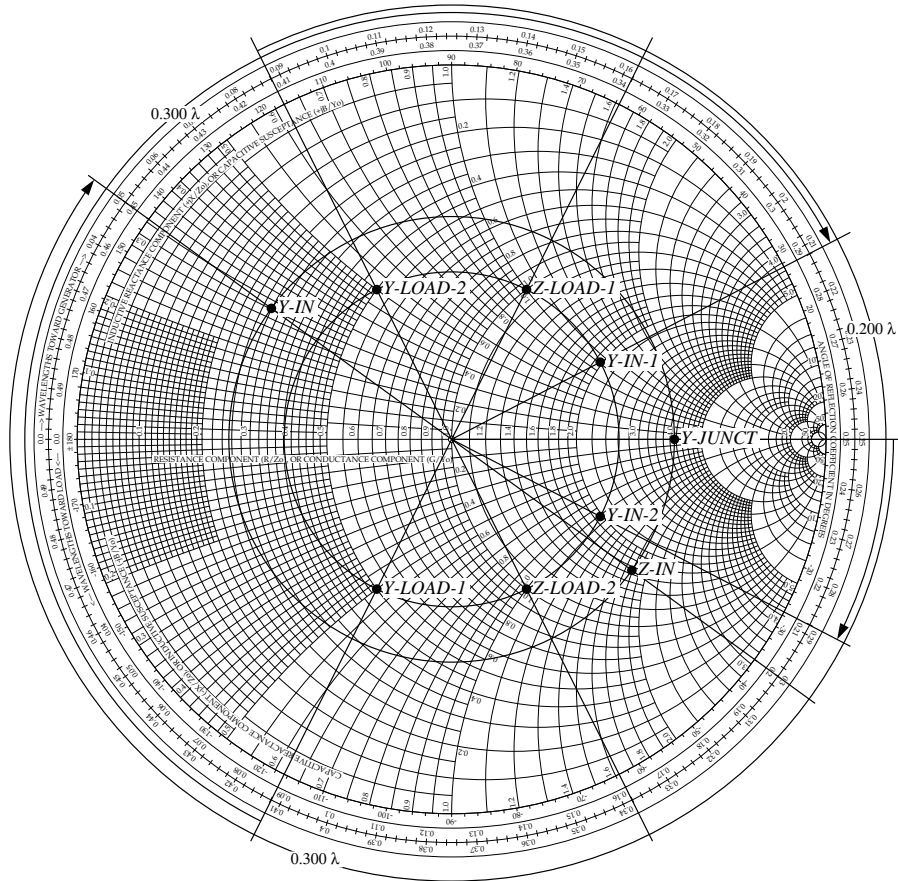

**Figure P2.72:** (a) Circuit of Problem 2.72.



**Figure 2.72:** (b) Solution of Problem 2.72.

**Solution:** Refer to Fig. P2.72(b).

$$z_1 = \frac{Z_1}{Z_0} = \frac{50 + j50 \, \Omega}{50 \, \Omega} = 1 + j1$$

and is at point *Z-LOAD-1*.

$$z_2 = \frac{Z_2}{Z_0} = \frac{50 - j50 \, \Omega}{50 \, \Omega} = 1 - j1$$

and is at point *Z-LOAD-2*. Since at the junction the lines are in parallel, it is advantageous to solve the problem using admittances.  $y_1$  is point *Y-LOAD-1*, which is at  $0.412\lambda$  on the WTG scale.  $y_2$  is point *Y-LOAD-2*, which is at  $0.088\lambda$  on the WTG scale. Traveling  $0.300\lambda$  from *Y-LOAD-1* toward the generator one obtains the

input admittance for the upper feed line, point  $Y-IN-1$ , with a value of  $1.97 + j1.02$ . Since traveling  $0.700\lambda$  is equivalent to traveling  $0.200\lambda$  on any transmission line, the input admittance for the lower line feed is found at point  $Y-IN-2$ , which has a value of  $1.97 - j1.02$ . The admittance of the two lines together is the sum of their admittances:  $1.97 + j1.02 + 1.97 - j1.02 = 3.94 + j0$  and is denoted  $Y-JUNCT$ .  $0.300\lambda$  from  $Y-JUNCT$  toward the generator is the input admittance of the entire feed line, point  $Y-IN$ , from which  $Z-IN$  is found.

$$Z_{in} = z_{in}Z_0 = (1.65 - j1.79) \times 50 \, \Omega = (82.5 - j89.5) \, \Omega.$$


---