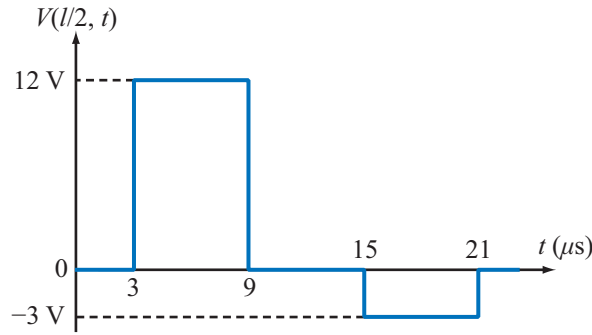


**Problem 2.82** In response to a step voltage, the voltage waveform shown in Fig. P2.82 was observed at the midpoint of a lossless transmission line with  $Z_0 = 50 \Omega$  and  $u_p = 2 \times 10^8$  m/s. Determine: (a) the length of the line, (b)  $Z_L$ , (c)  $R_g$ , and (d)  $V_g$ .



**Figure P2.82:** Circuit for Problem 2.82.

**Solution:**

(a) Since it takes  $3 \mu\text{s}$  to reach the middle of the line, the line length must be

$$l = 2(3 \times 10^{-6} \times u_p) = 2 \times 3 \times 10^{-6} \times 2 \times 10^8 = 1200 \text{ m}.$$

(b) From the voltage waveform shown in the figure, the duration of the first rectangle is  $6 \mu\text{s}$ , representing the time it takes the incident voltage  $V_1^+$  to travel from the midpoint of the line to the load and back. The fact that the voltage drops to zero at  $t = 9 \mu\text{s}$  implies that the reflected wave is exactly equal to  $V_1^+$  in magnitude, but opposite in polarity. That is,

$$V_1^- = -V_1^+.$$

This in turn implies that  $\Gamma_L = -1$ , which means that the load is a short circuit:

$$Z_L = 0.$$

(c) After  $V_1^-$  arrives at the generator end, it encounters a reflection coefficient  $\Gamma_g$ . The voltage at  $15 \mu\text{s}$  is composed of:

$$\begin{aligned} V &= V_1^+ + V_1^- + V_2^+ \\ &= (1 + \Gamma_L + \Gamma_L \Gamma_g) V_1^+ \\ \frac{V}{V_1^+} &= 1 - 1 - \Gamma_g \end{aligned}$$

From the figure,  $V/V_1^+ = -3/12 = -1/4$ . Hence,

$$\Gamma_g = \frac{1}{4},$$

which means that

$$R_g = \left( \frac{1 + \Gamma_g}{1 - \Gamma_g} \right) Z_0 = \left( \frac{1 + 0.25}{1 - 0.25} \right) 50 = 83.3 \, \Omega.$$

(d)

$$V_1^+ = 12 = \frac{V_g Z_0}{R_g + Z_0}$$

$$V_g = \frac{12(R_g + Z_0)}{Z_0} = \frac{12(83.3 + 50)}{50} = 32 \, \text{V}.$$