
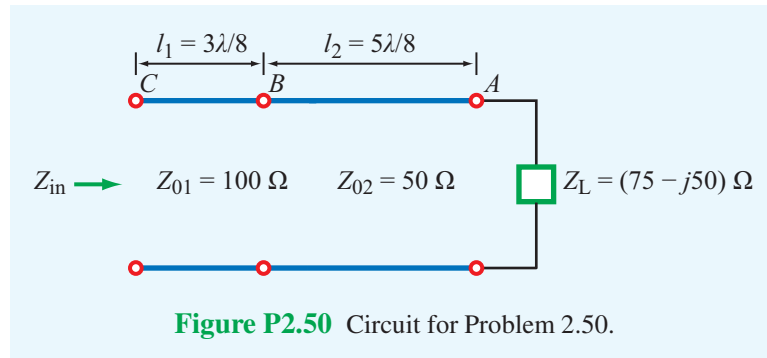


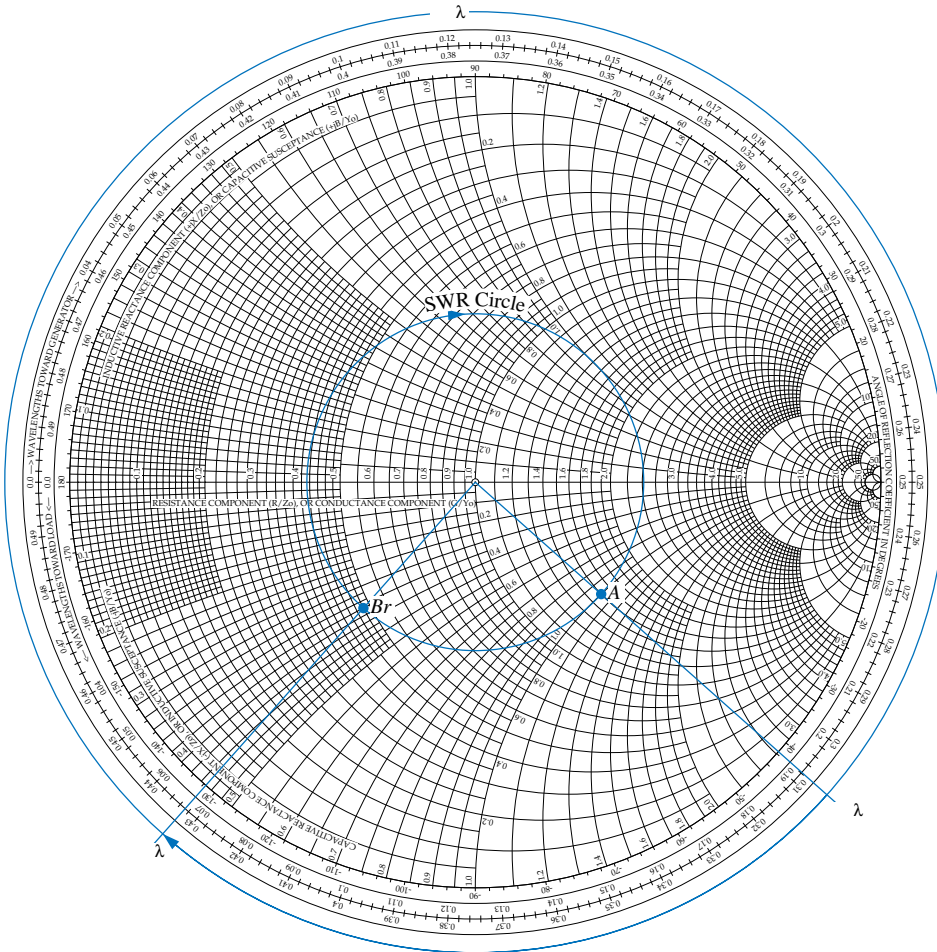**2.50** Use the Smith chart to determine the input impedance  $Z_{in}$  of the two-line configuration shown in Fig. P2.50.



**Solution:**



Smith Chart 1

Starting at point A, namely at the load, we normalize  $Z_L$  with respect to  $Z_{02}$ :


$$z_L = \frac{Z_L}{Z_{02}} = \frac{75 - j50}{50} = 1.5 - j1. \quad (\text{point A on Smith chart 1})$$

From point A on the Smith chart, we move on the SWR circle a distance of  $5\lambda/8$  to point  $B_r$ , which is just to the right of point B (see figure). At  $B_r$ , the normalized input impedance of line 2 is:

$$z_{in2} = 0.48 - j0.36 \quad (\text{point } B_r \text{ on Smith chart})$$

Next, we unnormalize  $z_{in2}$ :
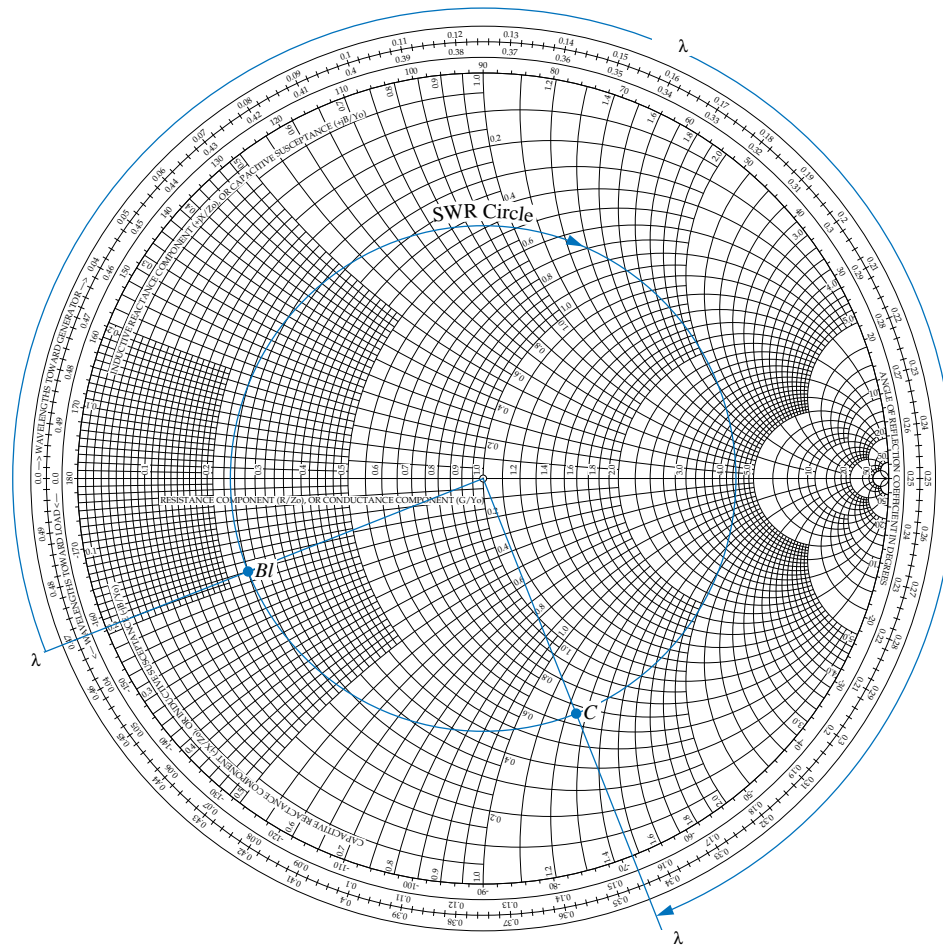
$$Z_{in2} = Z_{02} z_{in2} = 50 \times (0.48 - j0.36) = (24 - j18) \Omega.$$



Smith Chart 2

To move along line 1, we need to normalize with respect to  $Z_{01}$ . We shall call this  $z_{L1}$ :

$$z_{L1} = \frac{Z_{in2}}{Z_{01}} = \frac{24 - j18}{100} = 0.24 - j0.18 \quad (\text{point } B_\ell \text{ on Smith chart 2})$$

After drawing the SWR circle through point  $B_\ell$ , we move  $3\lambda/8$  towards the generator, ending up at point C on Smith chart 2. The normalized input impedance of line 1 is:

$$z_{in} = 0.66 - j1.25$$

which upon unnormalizing becomes:

$$Z_{in} = (66 - j125) \Omega.$$