

**2.36** A lossless transmission line is terminated in a short circuit. How long (in wavelengths) should the line be for it to appear as an open circuit at its input terminals?

**Solution:** From Eq. (2.84),  $Z_{\text{in}}^{\text{sc}} = jZ_0 \tan \beta l$ . If  $\beta l = (\pi/2 + n\pi)$ , then  $Z_{\text{in}}^{\text{sc}} = j\infty (\Omega)$ . Hence,

$$l = \frac{\lambda}{2\pi} \left( \frac{\pi}{2} + n\pi \right) = \frac{\lambda}{4} + \frac{n\lambda}{2}.$$

This is evident from Figure 2.19(d).

---