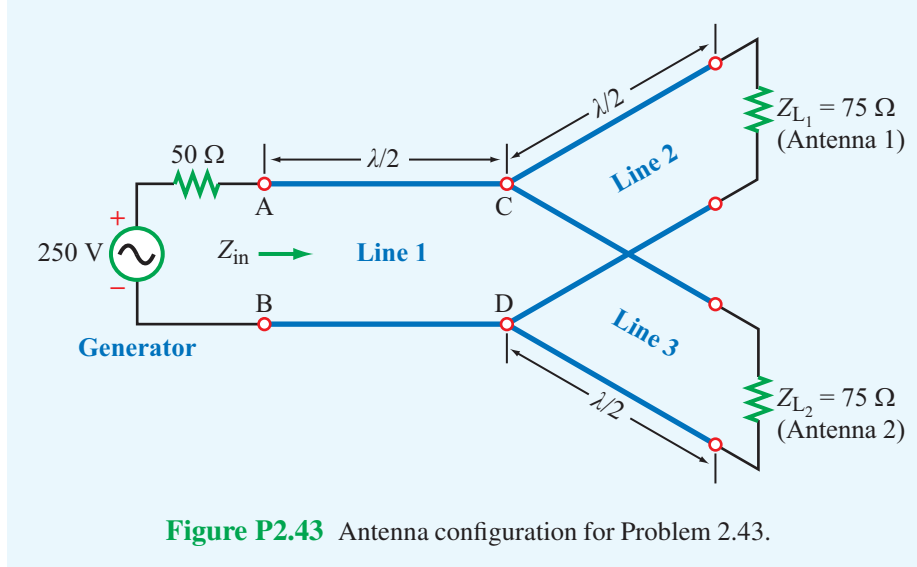


2.43 If the two-antenna configuration shown in Fig. P2.43 is connected to a generator with $\tilde{V}_g = 250$ V and $Z_g = 50$ Ω , how much average power is delivered to each antenna?



Solution: Since line 2 is $\lambda/2$ in length, the input impedance is the same as $Z_{L_1} = 75$ Ω . The same is true for line 3. At junction C–D, we now have two 75- Ω impedances in parallel, whose combination is $75/2 = 37.5$ Ω . Line 1 is $\lambda/2$ long. Hence at A–C, input impedance of line 1 is 37.5 Ω , and

$$\tilde{I}_i = \frac{\tilde{V}_g}{Z_g + Z_{in}} = \frac{250}{50 + 37.5} = 2.86 \quad (\text{A}),$$

$$P_{in} = \frac{1}{2} \Re[\tilde{I}_i \tilde{V}_i^*] = \frac{1}{2} \Re[\tilde{I}_i \tilde{I}_i^* \tilde{Z}_{in}^*] = \frac{(2.86)^2 \times 37.5}{2} = 153.37 \quad (\text{W}).$$

This is divided equally between the two antennas. Hence, each antenna receives $\frac{153.37}{2} = 76.68$ (W).