

2.5 For a parallel-plate transmission line, the line parameters are given by:

$$\begin{aligned}R' &= 2 \quad (\Omega/\text{m}), \\L' &= 335 \quad (\text{nH}/\text{m}), \\G' &= 0, \\C' &= 344 \quad (\text{pF}/\text{m}).\end{aligned}$$

Find α , β , u_p , and Z_0 at 1 GHz.

Solution: At 1 GHz, $\omega = 2\pi f = 2\pi \times 10^9$ rad/s. Application of (2.22) gives:

$$\begin{aligned}\gamma &= \sqrt{(R' + j\omega L')(G' + j\omega C')} \\&= [(2 + j2\pi \times 10^9 \times 335 \times 10^{-9})(0 + j2\pi \times 10^9 \times 344 \times 10^{-12})]^{1/2} \\&= [(2 + j2100)(j2.2)]^{1/2} \\&= 48e^{j89.97^\circ} = 0.023 + j48.\end{aligned}$$

Hence,

$$\begin{aligned}\alpha &= 0.023 \text{ Np/m}, \\ \beta &= 48 \text{ rad/m}.\end{aligned}$$

$$\begin{aligned}u_p &= \frac{\omega}{\beta} = \frac{2\pi f}{\beta} = \frac{2\pi \times 10^9}{48} = 1.31 \times 10^8 \text{ m/s}. \\Z_0 &= \left[\frac{R' + j\omega L'}{G' + j\omega C'} \right]^{1/2} \\&= \left[\frac{2100e^{j89.95^\circ}}{2.2e^{j90^\circ}} \right]^{1/2} \\&= \left[954e^{-j0.05^\circ} \right]^{1/2} \\&= 31e^{-j0.025^\circ} \approx (31 - j0.01) \Omega.\end{aligned}$$
