

2.52 A lossless $50\ \Omega$ transmission line is terminated in a load with $Z_L = (50 + j25)\ \Omega$. Use the Smith chart to find the following:

- (a) The reflection coefficient Γ .
- (b) The standing-wave ratio.
- (c) The input impedance at 0.35λ from the load.
- (d) The input admittance at 0.35λ from the load.
- (e) The shortest line length for which the input impedance is purely resistive.
- (f) The position of the first voltage maximum from the load.

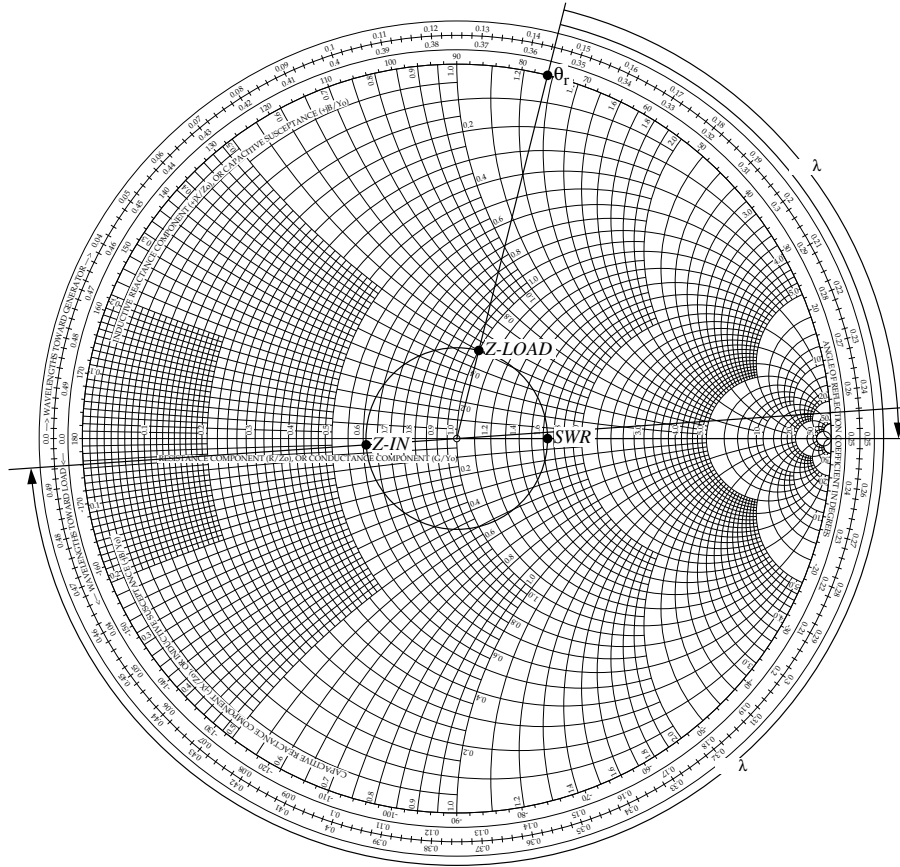


Figure P2.52: Solution of Problem 2.52.

Solution: Refer to Fig. P2.52. The normalized impedance

$$z_L = \frac{(50 + j25) \Omega}{50 \Omega} = 1 + j0.5$$

is at point **Z-LOAD**.

(a) $\Gamma = 0.24 \exp j76.0^\circ$ The angle of the reflection coefficient is read of that scale at the point θ_r .

(b) At the point **SWR**: $S = 1.64$.

(c) Z_{in} is 0.350λ from the load, which is at 0.144λ on the wavelengths to generator scale. So point **Z-IN** is at $0.144\lambda + 0.350\lambda = 0.494\lambda$ on the WTG scale. At point **Z-IN**:

$$Z_{in} = z_{in}Z_0 = (0.61 - j0.022) \times 50 \Omega = (30.5 - j1.09) \Omega.$$

(d) At the point on the SWR circle opposite *Z-IN*,

$$Y_{\text{in}} = \frac{y_{\text{in}}}{Z_0} = \frac{(1.64 + j0.06)}{50 \, \Omega} = (32.7 + j1.17) \, \text{mS}.$$

(e) Traveling from the point *Z-LOAD* in the direction of the generator (clockwise), the SWR circle crosses the $x_L = 0$ line first at the point *SWR*. To travel from *Z-LOAD* to *SWR* one must travel $0.250\lambda - 0.144\lambda = 0.106\lambda$. (Readings are on the wavelengths to generator scale.) So the shortest line length would be 0.106λ .

(f) The voltage max occurs at point *SWR*. From the previous part, this occurs at $z = -0.106\lambda$.
