
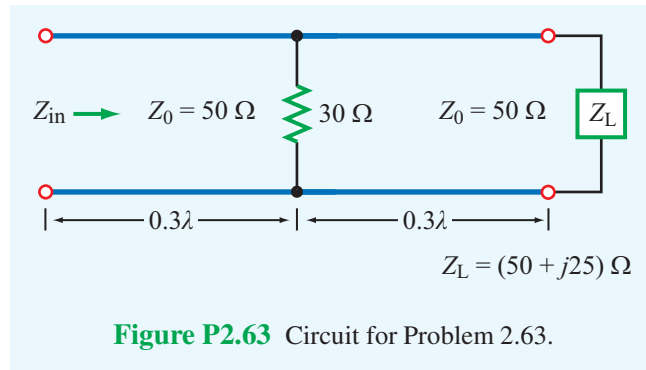


**2.63** A  $50\text{-}\Omega$  lossless line  $0.6\lambda$  long is terminated in a load with  $Z_L = (50 + j25)\text{ }\Omega$ . At  $0.3\lambda$  from the load, a resistor with resistance  $R = 30\text{ }\Omega$  is connected as shown in Fig. P2.63. Use the Smith chart to find  $Z_{in}$ .

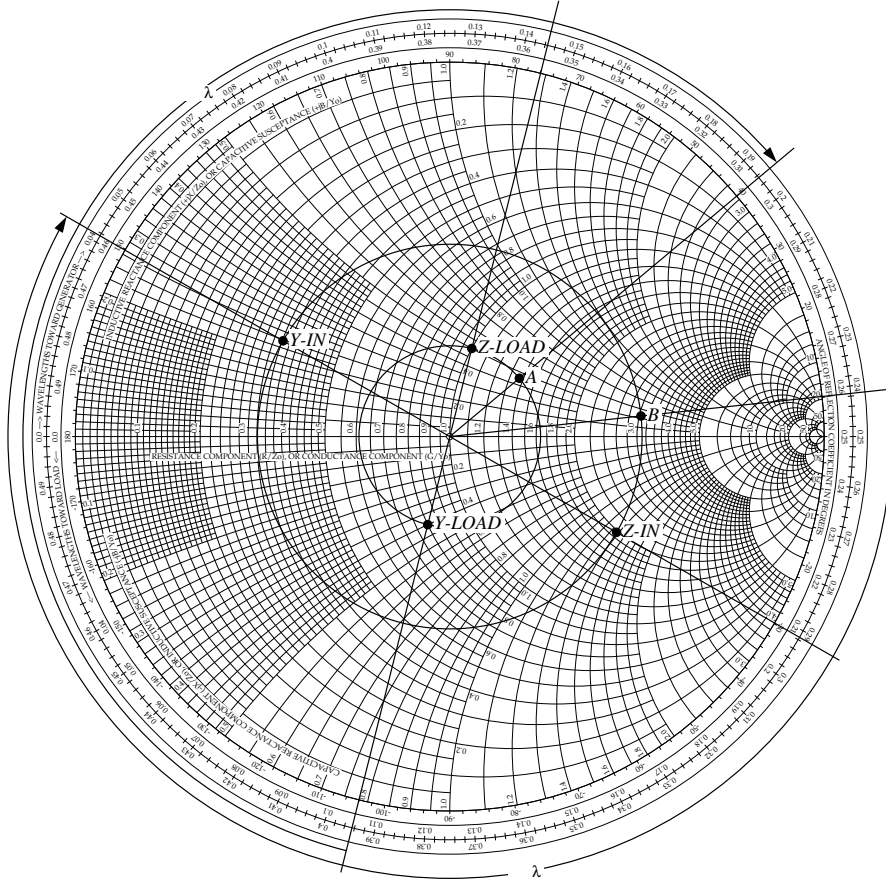



**Figure P2.63:** (b) Solution of Problem 2.63.

**Solution:** Refer to Fig. P2.63(b). Since the  $30\text{-}\Omega$  resistor is in parallel with the input impedance at that point, it is advantageous to convert all quantities to admittances.

$$z_L = \frac{Z_L}{Z_0} = \frac{(50 + j25)\ \Omega}{50\ \Omega} = 1 + j0.5$$

and is located at point *Z-LOAD*. The corresponding normalized load admittance is at point *Y-LOAD*, which is at  $0.394\lambda$  on the WTG scale. The input admittance of the load only at the shunt conductor is at  $0.394\lambda + 0.300\lambda - 0.500\lambda = 0.194\lambda$  and is denoted by point *A*. It has a value of

$$y_{inA} = 1.37 + j0.45.$$

The shunt conductance has a normalized conductance

$$g = \frac{50 \, \Omega}{30 \, \Omega} = 1.67.$$

The normalized admittance of the shunt conductance in parallel with the input admittance of the load is the sum of their admittances:

$$y_{inB} = g + y_{inA} = 1.67 + 1.37 + j0.45 = 3.04 + j0.45$$

and is located at point  $B$ . On the WTG scale, point  $B$  is at  $0.242\lambda$ . The input admittance of the entire circuit is at  $0.242\lambda + 0.300\lambda - 0.500\lambda = 0.042\lambda$  and is denoted by point  $Y-IN$ . The corresponding normalized input impedance is at  $Z-IN$  and has a value of

$$z_{in} = 1.9 - j1.4.$$

Thus,

$$Z_{in} = z_{in}Z_0 = (1.9 - j1.4) \times 50 \, \Omega = (95 - j70) \, \Omega.$$

---