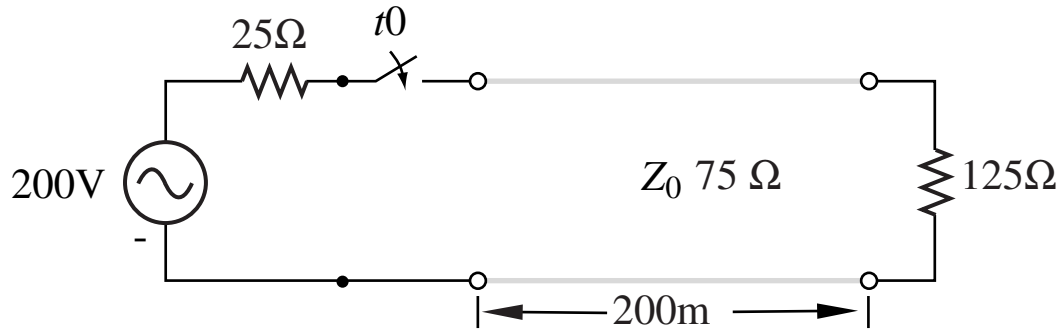


**2.81** A generator circuit with  $V_g = 200$  V and  $R_g = 25\ \Omega$  was used to excite a  $75\ \Omega$  lossless line with a rectangular pulse of duration  $\tau = 0.4\ \mu\text{s}$ . The line is 200 m long, its  $u_p = 2 \times 10^8$  m/s, and it is terminated in a load  $R_L = 125\ \Omega$ .

- (a) Synthesize the voltage pulse exciting the line as the sum of two step functions,  $V_{g_1}(t)$  and  $V_{g_2}(t)$ .
- (b) For each voltage step function, generate a bounce diagram for the voltage on the line.
- (c) Use the bounce diagrams to plot the total voltage at the sending end of the line.

**Solution:**



**Figure P2.81** (a) Circuit for Problem 2.81.

- (a) pulse length =  $0.4\ \mu\text{s}$ .

$$V_g(t) = V_{g_1}(t) + V_{g_2}(t),$$

with


$$V_{g_1}(t) = 200U(t) \quad (\text{V}),$$

$$V_{g_2}(t) = -200U(t - 0.4\ \mu\text{s}) \quad (\text{V}).$$

- (b)

$$T = \frac{l}{u_p} = \frac{200}{2 \times 10^8} = 1\ \mu\text{s}.$$

We will divide the problem into two parts, one for  $V_{g_1}(t)$  and another for  $V_{g_2}(t)$  and then we will use superposition to determine the solution for the sum. The solution for

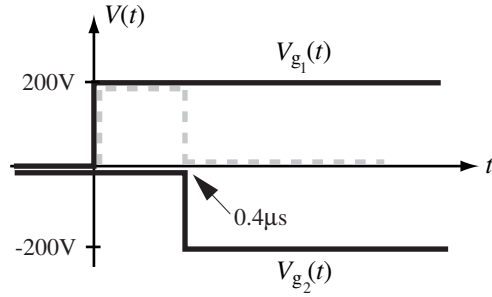

**Figure P2.81** (b) Solution of part (a).

$V_{g2}(t)$  will mimic the solution for  $V_{g1}(t)$ , except for a reversal in sign and a delay by  $0.4 \mu\text{s}$ .

For  $V_{g1}(t) = 200U(t)$ :


$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = \frac{25 - 75}{25 + 75} = -0.5,$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{125 - 75}{125 + 75} = 0.25,$$

$$V_1^+ = \frac{V_1 Z_0}{R_g + Z_0} = \frac{200 \times 75}{25 + 75} = 150 \text{ V},$$


$$V_\infty = \frac{V_g Z_L}{R_g + Z_L} = \frac{200 \times 125}{25 + 125} = 166.67 \text{ V}.$$

(i)  $V_1(0, t)$  at sending end due to  $V_{g1}(t)$ :

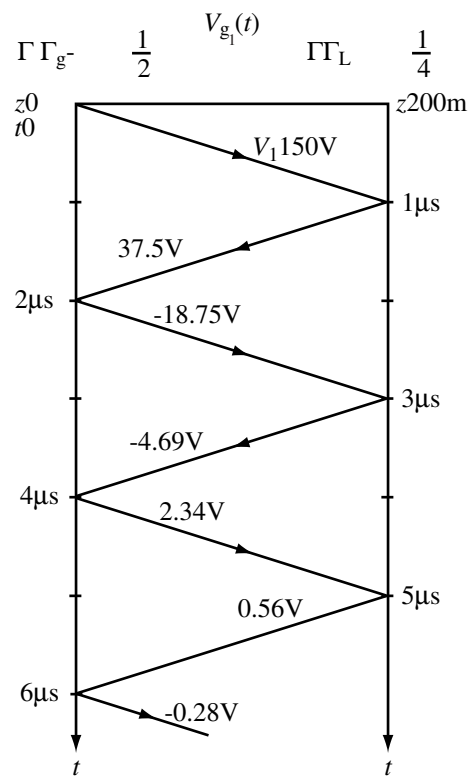

**Figure P2.81** (c) Bounce diagram for voltage in reaction to  $V_{g1}(t)$ .


(ii)  $V_2(0,t)$  at sending end due to  $V_{g2}(t)$ :

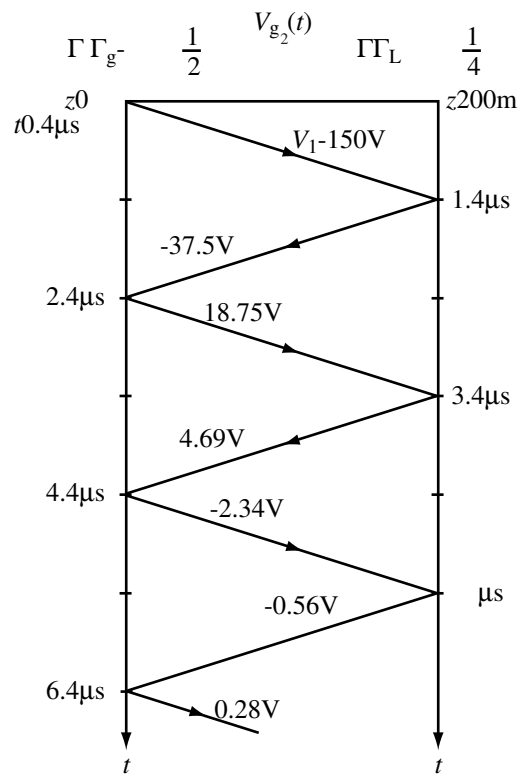


**Figure P2.81** (d) Bounce diagram for voltage in reaction to  $V_{g_2}(t)$ .

(b)

- (i)  $V_1(0, t)$  at sending end due to  $V_{g_1}(t)$ : see Fig. P2.81(e).
- (ii)  $V_2(0, t)$  at sending end: see Fig. P2.81(f).

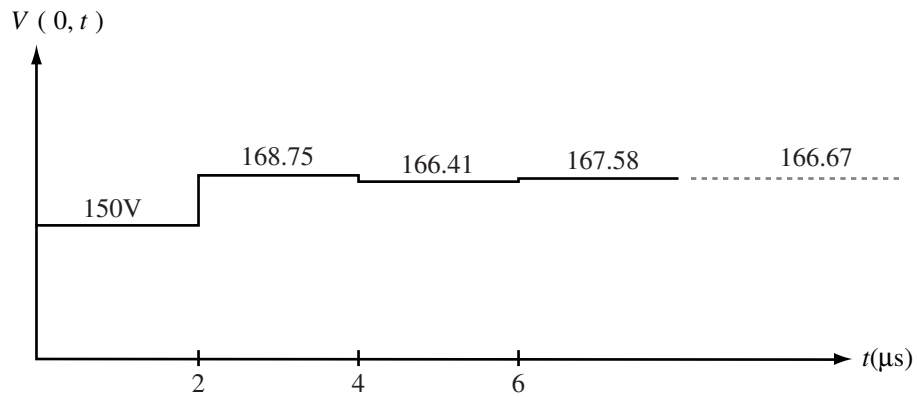


**Figure P2.81** (e)  $V_1(0, t)$ .

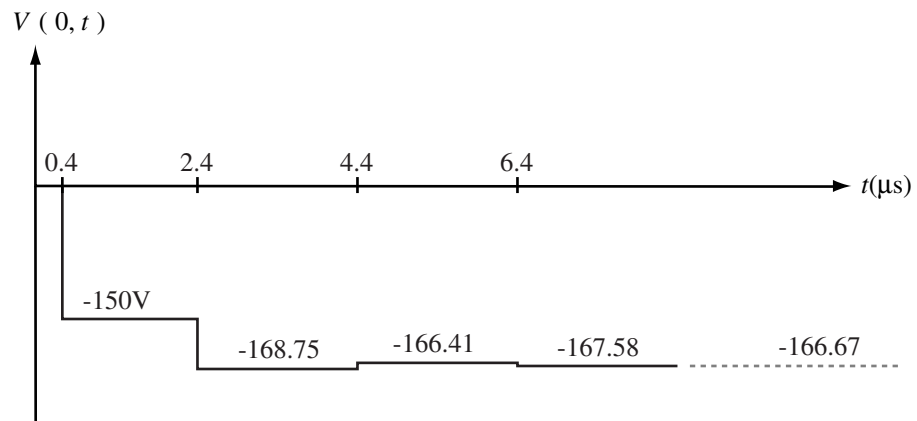

**Figure P2.81** (f)  $V_2(0, t)$ .

(iii) Net voltage  $V(0, t) = V_1(0, t) + V_2(0, t)$ : see Fig. P2.81(g).

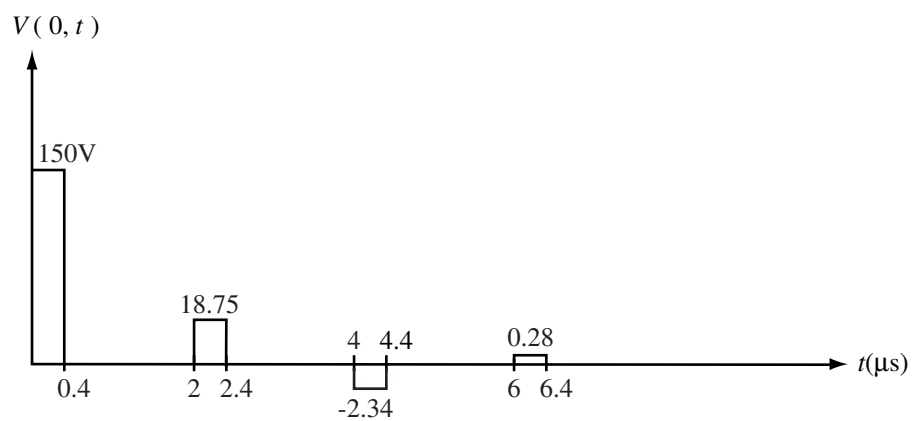

**Figure P2.81:** (g) Net voltage  $V(0, t)$ .

---